

Scimpy:
Sound **C**ard Based **I**mpedance
Measurements in **P**ython

Scott Howard

Last Revision: March 7, 2016

Copyright

© Copyright Scott Howard 2016

License

This work is licensed under the Creative Commons Attribution-ShareAlike 4.0 International License. To view a copy of this license, visit:

<http://creativecommons.org/licenses/by-sa/4.0/>



Contents

Preface	v
I Using Scimpy	1
1 Introduction	3
2 Usage	5
2.1 How to Connect Hardware	5
2.2 How to Use the Software	5
2.2.1 Taking Data	5
2.2.2 Interpreting Data	5
II Theory	7
3 Impedance	9
3.1 Electrical Impedance	10
3.2 Impedance Matching	11
3.2.1 Why Impedance Matching Doesn't Matter Any More	12
3.2.2 Why Impedance Matching Still Matters . .	14
3.2.3 Why Impedance <i>Measurements</i> Still Matter	15
3.3 Measuring Impedance	15
3.4 Crossover Circuits and Impedance	17

4	How Do Loudspeakers Work?	21
4.1	Electrical Model	22
4.2	Mechanical Model	23
4.3	Acoustical Model	24
4.4	Combined Model	31
5	Loudspeaker Box Design	37
5.1	Speaker with an Infinite Baffle	39
5.2	Sealed Box Enclosure	41
5.3	Vented/Ported/Bass-Reflex Enclosures	44
5.3.1	Fourth Order Butterworth Filter (B4)	
	$Q_{ts} = 0.383$	46
5.3.2	Fourth Order Chebyshev (C4)	
	$Q_{ts} > 0.383$	48
5.3.3	Third Order Quasi-Butterworth (QB3)	
	$Q_{ts} < 0.383$	51
5.4	Graphical Tool for Enclosure Design	53
5.4.1	Closed or Vented Box?	54
5.5	Group Delay?	55
5.6	Excursion and Power ratings?	55
5.7	Efficiency	55
5.8	Sound Power Level (SWL) and Sound Pressure Level (SPL)	56
5.9	Including effects of loss?	57
5.10	Computer Design:	57
5.10.1	Two-way Speaker Design	58
A	random stuff	59
A.1	excursion? Max power?	59
B	QB3, C4 Alignment Code	61

Preface

Purpose of this Book

DIY speaker building is a great combination of art and science that is accessible to a very wide population. Proper speaker design and characterization, however, typically require technical expertise and tools. The goal of this project is to provide an open-sourced platform to characterize electro-acousto-mechanical properties of speakers using a standard computer ADC/DAC, as well as a speaker design tool.

Commercial and closed-source software tools are available to characterize and aid design, but no open-source software and hardware projects exists. A few free tools exist, but are not open-source and are built on platforms that are no longer maintained. Open-source software projects enable users to add features & fix-bugs as needed as well as make long-term software maintenance possible even if the original author is no longer involved in the project.

About the Author

Dr. Scott Howard is a professor of electrical engineering at the University of Notre Dame. He received a PhD in Electrical Engineering from Princeton University and has preformed post-doctoral work at Princeton and Cornell University prior to appointment at Notre Dame.

At Notre Dame, Professor Howard has taught undergraduate-level “Electromagnetic Fields and Waves” and graduate courses in photonics and optics. He is the director of the Biomedical Photonics Research Laboratory and is funded by the National Science Foundation, US Department of Homeland Security, and US Department of Agriculture.

Dr. Howard is also a strong supporter of open-source software and hardware projects, as well as open and collaborative education. He is a Debian Developer and a contributor to several large projects including Arduino, LibreCAD, GNOME, and Ubuntu.

Part I

Using Scimpy

Chapter 1

Introduction

This is largely a presentation of the ideas from Thiele and Small's papers, we'll

“Hence the expression Butterworth box. However, in the spite of the phonetic similarity, butter boxes are not in general suitable as loudspeaker enclosures.”

– A. N. Thiele

test

test

Chapter 2

Usage

test

2.1 How to Connect Hardware

Headphones are typically 32 ohms, so want to use 20 ohm resistor to protect circuits?

line out? does it have enough current?

line in: 600-47 kOhms (low impedance) microphone, more sensitive but powered (need AC coupling?)

2.2 How to Use the Software

2.2.1 Taking Data

2.2.2 Interpreting Data

Part II

Theory

Chapter 3

Impedance

Modern amps have lots of current, digital feedback - is impedance important? probably not, except to help cross over maybe... Impedance measurements can get you info on internal parameters, help tune/design box for example!

Speaker impedance represents how much voltage will be needed to drive 1 A of current through the speaker voice coil. Higher resistance means that speaker response will drop, as it is harder to push current through it. Due to electrical, mechanical, and acoustical effects, impedance changes with frequency – thus changing how the speaker sounds. If speaker impedance drops too low, more current will be needed from the amplifier. Over-driving the speaker amplifier risks distortion and overheating the amplifier. Additionally, passive cross-over circuits (i.e., what splits the signal to tweeter and woofer) are designed to work with loads whose impedance do not change with frequency; poor impedance matching reduces cross-over performance

An “impedance matching” circuit can correct this poor performance. The circuit is designed such that the combined impedance of the speaker and circuit is the same for all frequencies, and thus avoiding signal distortion and amplifier damage.

Impedance circuits can be classified as active or passive. Active circuits are easier to design but are expensive and require ad-

ditional power. Passive circuits are cheaper, but a well designed circuit will perform as well as an active system. However, designing such circuits requires specialized equipment and software. Thus the motivation for this project: develop a widely available, easy-to-use tool to measure impedance and provide impedance matching circuit designs.

Section 3 will describe how to measure impedance. Section 4 will then build a model of loudspeaker performance.

3.1 Electrical Impedance

Voltage (V) and current (I) are related to each other through the following expressions describing resistors (with resistance R), capacitors (with capacitance C), and inductors (with inductance, L):

$$V = IR \qquad V = L \frac{\partial I}{\partial t} \qquad I = C \frac{\partial V}{\partial t} \qquad (3.1)$$

To understand their frequency response, we use generic time harmonic signals:

$$V = V_0 \cos(\omega t + \phi_V) = \Re\{\hat{V}e^{i\omega t}\} \qquad (3.2)$$

$$I = I_0 \cos(\omega t + \phi_I) = \Re\{\hat{I}e^{i\omega t}\} \qquad (3.3)$$

Where $\hat{V}(\omega) = V_0(\omega)e^{i\phi_V(\omega)}$ and $\hat{I}(\omega) = I_0(\omega)e^{i\phi_I(\omega)}$ are the phasor representation of voltage and current. Combining Equations 3.1 and 3.2 we can see that the phasor voltage and currents are proportional to each other by a factor of Z for each of the circuit elements.

$$\frac{\hat{V}}{\hat{I}} = Z_R = R \qquad Z_L = i\omega L \qquad Z_C = \frac{1}{i\omega C} \qquad (3.4)$$

Phasors allows us to easily calculate the relationship between voltage and current in complex circuits. For example, Figure 3.1 can be represented using phasor sources and complex impedances as in Figure 3.2.

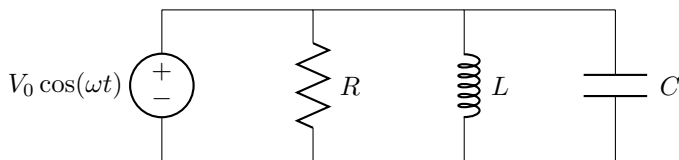


Figure 3.1: Example circuit

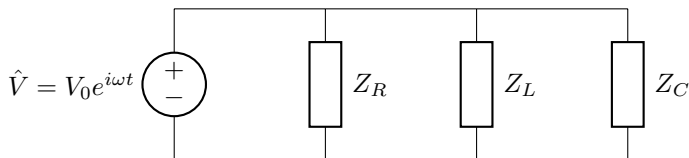


Figure 3.2: Example circuit with complex impedances

Using standard circuit analysis, you can calculate the current coming out of the voltage source by treating each circuit element as if it was a resistor.

$$Z = \left(\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right)^{-1} \quad (3.5)$$

$$\hat{I} = \hat{V} \left(\frac{Z_C Z_L + Z_R Z_L + Z_R Z_C}{Z_R + Z_C + Z_L} \right) \quad (3.6)$$

$$= V_0 e^{i\omega t} \left(\frac{L/C + i[-R/(\omega C) + \omega R L]}{R + i(\omega L - \omega/C)} \right) \quad (3.7)$$

Current, I , can now be found by taking the real part of \hat{I} .

3.2 Impedance Matching

Our challenge is to design a circuit that makes the impedance constant for all frequencies. For example, a speaker has an impedance $Z = R + Z_0$, which represents a DC ($\omega = 0$) resistance of R and a

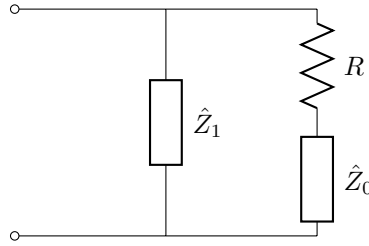


Figure 3.3: Speaker impedance matching

frequency dependant impedance Z_0 . to match impedance, a circuit with impedance Z_1 is added in parallel to the speaker, as depicted in Figure 3.3. The equivalent impedance is $Z = \frac{Z_1(R+Z_0)}{Z_1+Z_0+R}$. Setting $Z = R$ and solving for Z_1 yields:

$$Z_1 = R + \frac{R^2}{Z_0} \quad (3.8)$$

Equation 3.8 represents how we will design our impedance matching circuit. The circuit will consist of a resistor of resistance R in series with a circuit that is the “electric dual” of Z_0 scaled by R^2 . The electric dual of a circuit with impedance Z is defined as the circuit with impedance $Z' = 1/Z$.

1. Develop a circuit model for Z_0 (and thus the dual circuit model for Z'_0)
2. Measure $R + Z_0$ as a function of frequency to extract R and the values of the elements in the circuit model.

3.2.1 Why Impedance Matching Doesn't Matter Any More

Impedance matching is important (1) to ensure that the amplifier doesn't overwork itself and (2) to ensure that cross-over circuits are properly tuned.

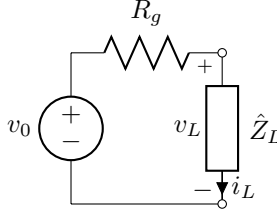


Figure 3.4: Amplifier Output Impedance

Amplifiers in Overdrive: Amplifiers can be modelled as voltage sources with some “output impedance” representing the resistance the amplified signal sees leaving the amplifier. This is depicted in Figure 3.4 where R_g is the output impedance of the amplifier, v_L is the voltage across the load, and \hat{Z}_L is the complex impedance of the load. The voltage seen by the speaker and the current delivered by the amp is:

$$\hat{v}_L = \hat{v}_0 \frac{\hat{Z}_L}{R_g + \hat{Z}_L} \quad \hat{i}_L = \frac{\hat{v}_L}{\hat{Z}_L} = \frac{\hat{v}_0}{R_g + \hat{Z}_L} \quad (3.9)$$

which illustrates two potential problems. (1) If $R_g > \hat{Z}_L$, then the voltage seen by the load (and thus audio response) will change with frequency since \hat{Z}_L is a function of frequency. (2) If $\Re\{\hat{Z}_L\}$ becomes low at a specific frequency, \hat{i}_L will increase rapidly with the risk of “burning out” the amplifier as all the amplifier power is dissipated solely in the amplifier internal load.

Originally, valve amplifiers (tube amps) were commonly used to amplify the small signal from audio sources, and exhibited R_g of 100s of Ω or more ($\gg \hat{Z}_L$). As such it was important that \hat{Z}_L remain real constant over all frequencies so that the tube does not burn out and performance remain consistent over all frequencies. Impedance matching achieved those goals. However, modern solid-state transistor-based amplifiers have near zero output impedance and therefore deliver the needed \hat{v}_L without impedance matching. In essence, low R_g allows solid-state amplifiers to output large \hat{i}_L in order to maintain $v_L = v_0$.

Impedance and Cross-Over Design: Impedance matching also helps cross-over design, as a flat and real load is assumed. However, if the cross-over frequency is chosen to be away from any resonance (such as choosing a cross-over frequency of an octave larger than the speaker resonance $2 \times f_s$), then impedance matching becomes less important as the load is essentially flat over the pass-band.

Time Average Power at the Speaker: On some DIY speaker forums, some point out the the average power delivered to the speaker *decreases* at speaker resonance if you use a solid-state amplifier, and then attribute this to a decrease in performance. While power delivered to the speaker does decrease at resonances, this does not necessarily translate to a decrease in output acoustic power. Output acoustic power is a function of v_L , not of the power delivered to the load, as will be seen in Chapter 4. A tube amp's large R_g makes the voltage delivered to the speaker vary as you approach resonance, which *does* distort the audio signal. A solid-state amplifier's \hat{v}_L is independent of \hat{Z}_L , and thus of frequency. In fact, this decrease in power is exactly what should happen: speaker efficiency is increasing (less current is needed for the same amount of mechanical deviation) therefore less current is required to achieve the same acoustic output power. The decrease in power delivered to the speaker at resonance is not the reason why solid-state amplifiers do not perform the same as tube amps, and in fact is one of the areas solid-state amplifiers may out-perform tube-amps.

3.2.2 Why Impedance Matching Still Matters

Valve/tube amplifiers are popular among audiophiles because they deliver a “warmth” unlike solid-state amps. Usage of these amplifiers in audio circuits requires impedance matching due to the large output impedance R_g . That said, some commercial tube amplifier systems know modern speakers are not commonly impedance matched. That’s why you see amplifiers using tube amplifiers as pre-amplifiers and solid-state amplifiers as buffers to drive speakers as an attempt to get the best of both worlds.

A well matched circuit ensures that maximum power is deliv-

ered to the load across all frequencies. Using impedance matching means the amplifier will not have to “work as hard,” and thus improve efficiency. If your amplifier is operating near the maximum output rating, it could be good to impedance match the system to ensure expected performance. However, it might be cheaper and easier to buy a bigger amplifier!

3.2.3 Why Impedance *Measurements* Still Matter

so you know speaker specs to design cab

3.3 Measuring Impedance

Impedance testing is actually relatively straight forward. A function generator creates voltage to a circuit that has a resistor (of accurately known resistance R_{test}) in series with the speaker. The function generator creates a sinusoidal voltage with constant amplitude V_0 at different frequencies ω . A volt meter measures the voltage across the test resistor, v_r , as a function of frequency ω . The generic test system is described in Figure 3.5. Speaker impedance can be found with the Equation 3.10, below:

$$\hat{v}_s = \frac{\hat{Z}_s V_0}{R_{test} + \hat{Z}_s} \quad \hat{i}_s = \hat{i}_r = \frac{\hat{v}_r}{R_{test}} \quad \hat{Z}_s = \frac{\hat{v}_s}{\hat{i}_s} = R_{test} \left(\frac{V_0}{\hat{v}_r} - 1 \right) \quad (3.10)$$

All variables with carrots indicate complex numbers with a phase relative to the source, V_0 .

Equation 3.10 assumes the magnitude and phase of \hat{v}_1 can be measured relative to the phase of the source with, for example, an oscilloscope locked in to the frequency and phase of the voltage source. If you don’t have such a lock-in detection scheme (which few do), but do have time sensitive measurements (e.g., a sound card like we use in this project). You can rearrange Equation 3.10 to be:

$$\hat{Z}_s = R_{test} \left(\frac{V_0 - \hat{v}_r}{\hat{v}_r} \right) = R_{test} \left(\frac{\hat{v}_s}{\hat{v}_r} \right) \quad (3.11)$$

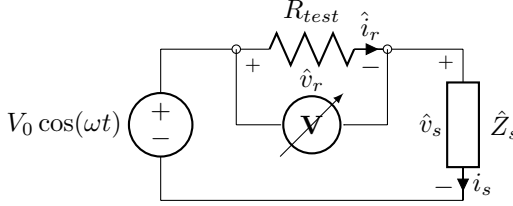


Figure 3.5: Typically described speaker impedance measurement (requires voltmeter to be locked-in to the source phase)

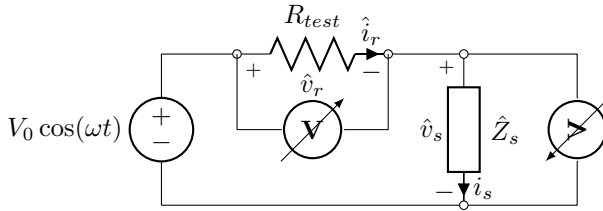


Figure 3.6: Speaker impedance matching (this project, no lock-in required)

which shows we need a another voltage meter to get \hat{v}_s . This is shown in Figure 3.6, and is the circuit this project uses to find \hat{Z}_s in Equation 3.11).

Commonly, time sensitive measurements are impractical as hobbyist typically only have multimeters, which can measure AC RMS. If only the RMS magnitude of AC voltage can be measured, then the magnitude of Z can be found as in Equation 3.12.

$$|\hat{Z}_s| = \frac{|v_s| R_{test}}{|v_r|} \quad (3.12)$$

Note: Equation 3.12 differs from some hobbyist impedance measurement techniques¹ which ignores the fact that phases of each of the voltages are not the same!

¹Sometimes incorrectly given as: $|Z_s| = R \left(\frac{|V_0|}{|v_r|} - 1 \right)$

Once \hat{Z} or $|\hat{Z}|$ is found for different frequencies ω , you can fit the data to the models in Section 4 to extract the values needed to make the impedance matching circuit.

3.4 Crossover Circuits and Impedance

Scott notes: Editorial Note About Directivity, Crossover Points & Driver Selection by Dr. Floyd Toole

A good sounding loudspeaker needs to have smooth and flat on-axis frequency response and similar performance as we move far off axis. We describe this in terms of directivity as a function of frequency, and although absolutely constant directivity is not necessary, smooth and gradually-changing directivity is a good objective. In deciding on the drivers to be used in a speaker system it is necessary to ensure that at crossover frequencies the drivers have closely matching directivities. This means that when the acoustic transition is made between, say, a woofer and a midrange, or a midrange and a tweeter, there is continuity in the directional sound radiation pattern. It is not sufficient just to have a good looking on-axis response. So, in addition to selecting drivers for their useable bandwidths and power handling capabilities, we need to pay attention to their directional radiation patterns. The most difficult transitions occur when the transducers involved are very different in size. Editorial Note by Steve Feinstein on Crossover Frequency Selection

A basic, ages-old but still true, rule of thumb states that a designer is usually safe when he crosses a driver over at double its resonant frequency. If a tweeter has an F_s of 1500 Hz, use a 3000 Hz crossover, minimum. If a midrange is 300 Hz, use 600 Hz.

Another good rule of thumb says, “18 dB down at resonance.” If a tweeter’s resonance is 1500 Hz, the voltage curve of the crossover should show the tweeter section being down 18 dB from “0 dB.” That kind of conservatism all but assures no tweeter burn-out.

This was the “rule” at a major speaker company I used to work at, and the engineers all hated it, because it was so conservative and resulted in very high tweeter crossover points. But we almost never lost a tweeter and our warranty costs were vanishingly low.

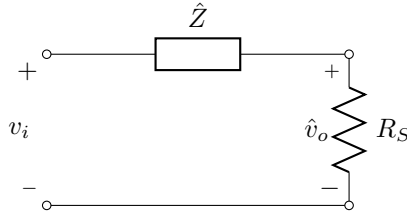


Figure 3.7: First order filter

‘Real world’ vs. ‘theory.’ from: <http://www.audioholics.com/loudspeaker-design/crossovers>

START HERE:

Cross-over circuits are needed to separate the sound signal into high and low frequency components. Ideally for dipole speakers, you want a “switch” that sends low frequency below some cross-over frequency ω_c only to the woofer and higher frequencies only to the tweeter. Practically, some leakage will occur in separating the signals such that some low frequencies will end up at the tweeter, and high at the woofer. These negative effects define the engineering problem.

Cross-over circuits are either classified as active (powered) or passive (unpowered). *Active cross-overs* use operational amplifiers (op amps) that can drive loads with complex \hat{Z} uniformly across all frequencies and thus do not need impedance matching circuits. However, they tend to be a bit complicated, expensive, and require additional power. *Passive cross-overs* are cheaper, simpler, and don’t require extra power – but do require extra care in design to achieve the same theoretical performance as active cross-overs. Since we have the tools to properly design cross-overs, we will consider passive cross-overs.

After building the impedance matching circuit, we need to build a circuit that separates the low and high frequency components. Next, the simplest electric filter is an inductor or a capacitor in series with a resistor to make a low-pass and high-pass filter, respectively, as in Figure 3.7.

The transfer function (\hat{H} , the ratio of output to input voltage)

can be found for $\hat{Z} = i\omega L$ and $\hat{Z} = \frac{1}{i\omega C}$

$$\hat{H}_{LP}(\omega) = \left(1 + \frac{i\omega L}{R}\right)^{-1} = \left(1 + \frac{\omega^2}{\omega_c^2}\right)^{-\frac{1}{2}} e^{\tan^{-1}\left(\frac{\omega}{\omega_c}\right)} \quad (3.13)$$

$$\hat{H}_{HP}(\omega) = \left(1 + \frac{1}{i\omega RC}\right)^{-1} = \left(1 + \frac{\omega_c^2}{\omega^2}\right)^{-\frac{1}{2}} e^{\tan^{-1}\left(\frac{\omega_c}{\omega}\right)} \quad (3.14)$$

L and C are picked for a given cross-over frequency such that $L = \frac{R}{\omega_c}$ and $C = \frac{1}{R\omega_c}$. Note that the sum of both speaker outputs $\hat{H}_{LP}(\omega) + \hat{H}_{HP}(\omega) = 1$ for all frequencies! That means that the signal is transferred perfectly in amplitude (volume) and phase (audible delay) at every frequency. However, each driver demonstrates a group phase delay ($\partial\phi/\partial\omega$) in the pass-bands, so how can it appear to have zero-phase? Well, it's a bit of a trick in that the system "uses" *both* speakers to correct for this variable delay as a function of frequency. Low frequencies coming from the woofer have small delay (phase), while those low frequencies in the tweeter have a lot of delay. As frequency increases, woofer delay increases and tweeter delay decreases. The apparent phase (delay) is unchanged. This is not ideal as it relies on driving your tweeter lower than designed (risking overheating and damage) and your woofer higher than intended (excited standing waves/nodes within the woofer driver which degrades sound quality). Therefore, high-order filters are preferred.

High order filters (i.e., ones that separate tweeter and woofer signals better) can be used, but requires more parts. See, for example, Linkwitz-Riley (LR) filters for a high-order filter. The LR2 filter design is shown in Figure 3.8. Choosing $Z_1 = Z_2$ and $R_s = R_1$, you can calculate transfer functions in the Maxima computer algebra system (left for the reader):

You can see that the LR2 filter has many positive features compared to our simple filter (1) Faster roll-off (12 dB/octave versus 6 dB/octave) – better separation of frequencies to protect the drivers. (2) Phase is flat (low group delay) in the pass-bands. There is, however, some group delay around cross-over. (3) Constant phase offset between woofer & tweeter for all frequencies. Offset is 180° , so you need to wire one of the drivers backwards

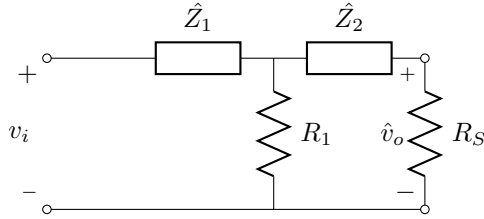


Figure 3.8: Linkwitz-Riley Second Order Filter (LR2)

(negative polarity). (4) Like our simple system, choose $L = R/\omega_c$ and $C = 1/(\omega_c R)$.

Chapter 4

How Do Loudspeakers Work?

This section describes and summarizes a common mathematical model for aiding loudspeaker design. This approach was developed by the pioneers Neville Thiele of the Australian Broadcasting Commission, and Richard H. Small of the University of Sydney, and the parameters are commonly known as the “Thiele/Small Parameters.”

A loudspeaker converts electrical signals to sound waves by using the signal electrical voltage to drive a current which applies a force on a speaker membrane that in turn pushes a volume air. This pushed volume of air propagates as a sound wave to the listener.

To understand this process, we will break down the electrical, mechanical, and acoustical systems individually. We will also describe how each are connected. From the individual system models and our understanding of how they are connected, we will finally integrate them in to a complete single model which can be used to describe how loudspeakers work.

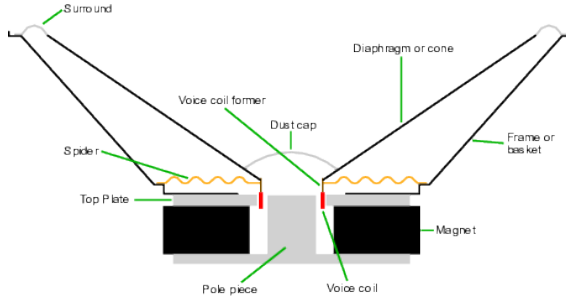


Figure 4.1: Loudspeaker Driver

4.1 Electrical Model

A loudspeaker driver is fundamentally a system that translates electrical current to air motion. Current through a coil of wires (called the voice coil) interacts with a permanent magnet, as described in Figure 4.1¹. Wire, itself, is a resistor; when coiled a wire is an inductor; and the time varying magnetic field created by an inductor induces “eddy currents” in nearby conductors which act as a resistor in parallel with the inductor. This electrical current can then be coupled to the mechanical vibrations (discussed in Section 4.2). The electrical model is thus described in Figure 4.2. Where R_{vc} is the DC resistance of the voice coil, L_{vc} is the inductance of the voice coil, \hat{Z}_e is the electrical impedance equivalent to the mechanical impedance due to the electrical-mechanical coupling, and R_{eddy} is the effective resistance due to eddy currents which is typically very high and frequently ignored in models. Finally, the current i_e is the current that couples to mechanical motion described by \hat{Z}_e as described in Section 4.2.

¹By Iain, png by Rohitbd [CC-BY-SA-3.0], via Wikimedia Commons

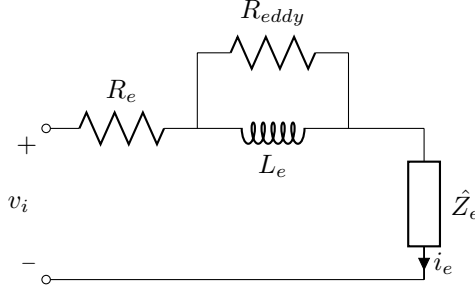


Figure 4.2: Electrical Model

4.2 Mechanical Model

Electric current is coupled to mechanical motion by the Lorentz Force equation:

$$\mathbf{F} = Q\mathbf{E} + Q\mathbf{v} \times \mathbf{B} = Q\mathbf{E} + Q\ell \mathbf{I} \times \mathbf{B} \quad (4.1)$$

Where F is force, Q is charge, v is velocity of the charge, and B is the magnetic field (i.e., the length of the coil), ℓ is length of the wire in the field, and I is the current. When current is moving in the wire, it exerts a force of

$$F = IB\ell \quad (4.2)$$

When a wire moves perpendicular to a magnetic field, carriers inside the wire feel a force of $F_B = QvB$. This force pushes electrons to one end of the wire, which creates a Coulomb force of $F_E = QE$. These two forces sum to zero, so $vB = -E$. This allows us to connect voltage across the coil, V , to velocity, v :

$$V = - \int E \, d\ell = \int vB \, d\ell = vB\ell \quad (4.3)$$

From Equations 4.2 and 4.3, electrical impedance can be found in terms of force F and v in a mechanical system:

$$\hat{Z}_e = \frac{V}{I} = \frac{v}{F} (B\ell)^2 \quad (4.4)$$

To continue with our model, we need to find the relationship between v and F , so we turn to Newton's law of motion and Hook's law for a dampened mass on a spring:

$$\sum F = M_{ms} \frac{d^2 x}{dt^2} \quad (4.5)$$

$$F - \frac{1}{C_{ms}} x = M_{ms} \frac{d^2 x}{dt^2} + R_{ms} \frac{dx}{dt} \quad (4.6)$$

$$F = M_{ms} \frac{dv}{dt} + R_{ms} v + \frac{1}{C_{ms}} \int v dt \quad (4.7)$$

$$F(\omega) = i\omega M_{ms} v + R_{ms} v + \frac{1}{i\omega C_{ms}} v \quad (4.8)$$

where M_{ms} is the mass of the diaphragm and coil (and acoustic mass), C_{ms} is the compliance of the suspension (i.e., $1/k$ of Hooke's Law), and R_{ms} represents the coefficient of friction (mechanical resistance to motion). From Equation 4.8, you can see that we can actually model mechanical systems as electrical circuits. In such a circuit, voltages represent force, current represents velocity, inductance is mass, electrical resistance is mechanical resistance, and capacitance is compliance. Mechanical impedance, is thus:

$$\hat{Z}_m = \frac{F}{v} \quad \hat{Z}_e = \hat{Z}_m^{-1} (B\ell)^2 \quad (4.9)$$

Equation 4.9 shows that if we represent our mechanical system as a mechanical circuit and find the mechanical impedance, the equivalent electric circuit is the dual of the mechanical circuit scaled by $(B\ell)^2$.

The mechanical system in Equation 4.8 describes the speaker in vacuum, that is without interacting with air. The driver will push a volume of air to generate sound, and thus is an additional complex component in our circuit. Therefore the complete mechanical circuit is described in Figure 4.3.

4.3 Acoustical Model

From Section 4.2, we found a way to find the velocity the diaphragm will move as a function of input current. The moving

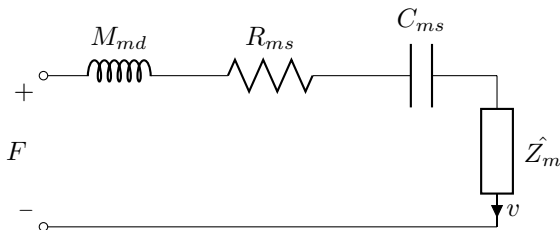


Figure 4.3: Mechanical Model

diaphragm will push air and create a pressure wave, which is what we will hear. The speaker diaphragm pushes the following V of air per second:

$$Q = S_d v \quad (4.10)$$

Where Q is the volume velocity, v is diaphragm velocity as found in Section 4.2, and S_d is the area of the driver diaphragm. Also, it is possible to convert between mechanical and acoustic impedances by using the speaker diaphragm area S_d :

$$Z_m = \frac{F}{v} = \frac{p S_d}{Q/S_d} = S_d^2 Z_a \quad (4.11)$$

When mounted in a speaker enclosure, the air pushed/pulled from the front of the diaphragm radiates as sound waves while the air pushed/pulled from the back of the driver is shielded from the listener. This is because the sound waves from the back are perfectly out of phase from the front, and thus will lead to audio nulls in the room.

To stop this interference, the air pushed/pulled from the back of the driver is typically enclosed in a box. Through some acoustic tricks, one can invert the phase of the rear acoustic waves by the use of a “port” or ”bass reflex” which is essentially a tube opening up to the space the inside of the speaker enclosure. See Figure 4.4 ².

²By Rohitbd, original by Melancholie.

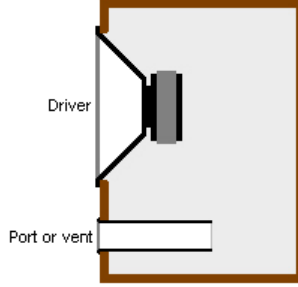


Figure 4.4: Bass Reflex Speaker or Vented Speaker Enclosure

We will consider this vented enclosure as our model since it is an extremely common enclosure and the model can be easily adapted for other enclosures. First, we must find what the change in pressure p is caused by Q . We know that pressure is increased per percent change in gas volume in the box V_B by a factor of compressibility⁻¹ = ρc^2 :

$$p = \rho c^2 \frac{\Delta V_B}{V_B} = \rho c^2 \frac{\int Q_B dt}{V_B} \quad (4.12)$$

$$\hat{p} = \frac{\rho c^2}{i\omega V_B} \hat{Q}_B = \frac{1}{i\omega C_{ab}} \hat{Q}_B \quad (4.13)$$

where Q_B is the volume velocity in to the box, ρ is gas density, c is the speed of sound, and $C_{ab} = \frac{V_B}{\rho c^2}$ is the acoustic capacitance of the box.

This increase of pressure inside the box will cause air flow in the port or vent, and acoustic radiation away from the vent. This air flow in a vent with area A_v , length ℓ_v , volume V_v will cause a pressure drop due to Newton's Law:

$$F = m \frac{dv}{dt} + \frac{\mu V_v}{\kappa} v \quad (4.14)$$

$$p = \rho \frac{\ell_v}{A_v} \frac{dQ_v}{dt} + \frac{\mu \ell_v}{\kappa A} v \quad (4.15)$$

$$\hat{p} = i\omega \rho \frac{\ell_v}{A_v} \hat{Q}_v + \frac{\mu \ell_v}{\kappa A_v} \hat{Q}_v \quad (4.16)$$

Term	Description	Usage
$L = \frac{\rho \ell}{A}$	Inertia of a volume of air	Speaker vent/port (L_{av})
$R = \frac{\mu \ell}{\kappa A}$	Resistance to laminar flow	Air leaking out the box (R_{al}); Air flow in acoustic filling material (R_{ab})
$C = \frac{V}{\rho c^2}$	How easily air can compress	Box compliance (C_{ab})

Table 4.1: Guide to Acoustic Impedance Terms

$$\hat{p} = i\omega L_{av} \hat{Q}_v + R_{av} \hat{Q}_v \quad (4.17)$$

where the second term is Darcy's law that describes Q in a porous medium *permeability* of κ and viscosity μ .

In theory, every time there is flow, acoustic inductance, resistance, and capacitance is present. Therefore, a generic element follows both Equation 4.13 and 4.17:

$$\hat{p} = i\omega L \hat{Q} + R \hat{Q} + \frac{1}{i\omega C} \hat{Q} \quad (4.18)$$

However, only one or two of the terms will typically dominate. To determine which to use, each can be calculated (effectively determining the Reynolds number). General rules to determine which effects are present are described in Table 4.1.

To account for air leakage out of the box, we can use Table 4.1 to describe the volume of air to flow leaking out of the box each second:

$$\frac{p}{R_{al}} = Q_l \quad (4.19)$$

Finally, we can get to acoustic radiation... that is sound! For this, we will find the relationship between volume velocity Q and pressure p at a radiation point (driver or bass vent). To do this, we start with the pressure wave equation:

$$\left(\nabla^2 - \frac{1}{c^2} \frac{\partial^2}{\partial t^2} \right) p = 0 \quad (4.20)$$

and assume a spherical wave solution of the form:

$$p = \Re \left\{ \frac{K}{r} e^{i(\omega t - kr)} \right\} \quad (4.21)$$

where K is an unknown constant and $k = \omega/c = 2\pi/\lambda$ (i.e., the spatial frequency of the wave). We know that at the port, we have volume velocity Q_0 , so we need to find K at the boundary. The easiest way to do this is to assume $Q = Q_0$ when r is equal to the radius of your opening a , assuming $a \ll \lambda/2\pi$. That basically places a spherical monopole in your opening³. Moving on assuming a time harmonic volume velocity $Q = \Re \left\{ \hat{Q}_0 e^{i\omega t} \right\}$ we can find Q from the surface of our spherical monopole with radius a :

$$Q_a = Av_a(t) = \frac{4\pi a^2}{2} v_a(t) \approx \hat{Q}_0 e^{i\omega t} \quad (4.22)$$

where Q_0 is the volume velocity inside the port. The velocity at radius a from the center of the port is thus:

$$v_a = \frac{1}{2\pi a^2} \hat{Q}_0 e^{i\omega t} \quad (4.23)$$

To make the connection between pressure and velocity, we can look to conservation of momentum. Momentum conservation says that the rate of momentum increase is equal to the force density f (N/m³) on a fluid.

$$F = m \frac{dv}{dt} \quad (4.24)$$

$$\int f dV = \int \rho dV \frac{dv}{dt} \quad (4.25)$$

$$f = \rho \frac{\partial v}{\partial t} \quad (4.26)$$

$$-\nabla p = \rho \frac{\partial}{\partial t} (\hat{v} e^{i\omega t}) \quad (4.27)$$

³This is an approximation, more formal analysis of acoustic radiation models the vent as a piston. The approach here still works pretty well at drawing some meaningful conclusions, nonetheless.

$$\frac{ikK}{r}e^{i(\omega t - kr)} + \frac{K}{r^2}e^{i(\omega t - kr)} = \rho i\omega \hat{v} e^{i\omega t} \quad (4.28)$$

$$\frac{kK}{\omega \rho r}e^{-ikr} - \frac{iK}{\omega \rho r^2}e^{-ikr} = \hat{v} \quad (4.29)$$

$$\frac{\hat{p}}{\rho c} \left(1 - \frac{i}{kr} \right) = \hat{v} \quad (4.30)$$

We now evaluate Equation 4.29 to find Q at $r = a$, that is at the output of the port where the area is a hemisphere pointing out to space:

$$\frac{krK}{\omega \rho r^2}e^{-ikr} - \frac{iK}{\omega \rho r^2}e^{-ikr} = \frac{1}{2\pi a^2}\hat{Q}_0 \quad (4.31)$$

$$K = \frac{\omega \rho}{2\pi(ka - i)}\hat{Q}_0 e^{ika} \quad (4.32)$$

Therefore:

$$p_{r=a} = \frac{\omega \rho \hat{Q}_0}{2\pi a(ka - i)}e^{i(\omega t - k(r-a))} \quad (4.33)$$

$$\hat{Z} = \frac{\hat{p}}{\hat{Q}} = \frac{\omega \rho}{2\pi r(ka - i)} = \frac{\omega^2 \rho}{2\pi c(k^2 a^2 + 1)} + \frac{i\rho \omega}{2\pi a(k^2 a^2 + 1)} \quad (4.34)$$

That is, the impedance a volume velocity of Q_0 feels at the output of the port, approximated by $r = a$. Now we consider $(ka)^2 \ll 1$ by assuming $\lambda \gg 2\pi a$:

$$\hat{Z}_{rad} = \frac{\omega^2 \rho}{2\pi c} + \frac{i\rho \omega \frac{a}{2}}{\pi a^2} = R_{rad} + i\omega L_{rad} \quad L_{rad} = \frac{\rho \frac{a}{2}}{\pi a^2} \quad (4.35)$$

There is a radiative (power transmitted as sound) and inductive (air mass being pushed) components, which follow forms very similar to Table 4.1. Inductance for example, is modelled as extending the vent tube (with radius a_v and area πa_v^2) by a length $a_v/2$ or increasing the mass of the diaphragm by $\frac{\rho S_d a_d}{2}$ (with diaphragm radius of a_d and area S_d). This additional mass is commonly lumped in with the diaphragm mass $M_{ms} = M_{md} + S_d^2 L_{rad}$ or acoustic mass $L_{avt} = L_{av} + L_{rad}$.

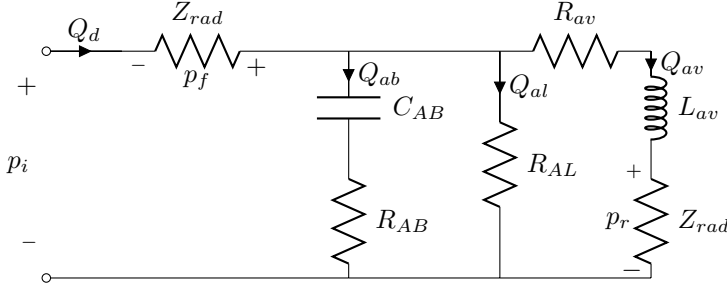


Figure 4.5: Acoustic Circuit Model

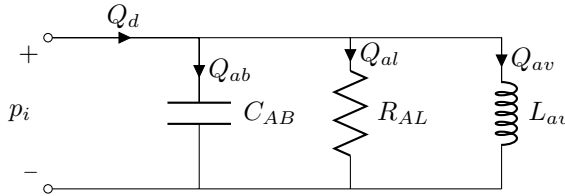


Figure 4.6: Common Simplified Acoustic Circuit Model

We now have all the tools to model the acoustic system as a circuit. When the speaker driver moves with velocity v (as determined in Section 4.2, It will create a $Q_d = v_d S_d$. This Q_d radiates as sound and also drives air into the enclosure box Q_b . The increased volume of air in the box increases the pressure in the box. Increased pressure drives air to leak out of the box; and the box increase in box pressure causes flow and radiation out of the vented port. This complete model is described in Figure 4.5. The forward speaker radiation p_f is in reverse polarity to indicate the radiation is 180° out of phase from Q_d since Q_d is defined as positive when pushing air in to the enclosure. R_{ab} is included to account for pressure loss due to filling material in the enclosure. Figure 4.6 shows a commonly employed simplified model; we will see in Section 4.4 that several terms will be able to be combined to yield this simplified model.

bass reflect out of phase!? yes/no!?

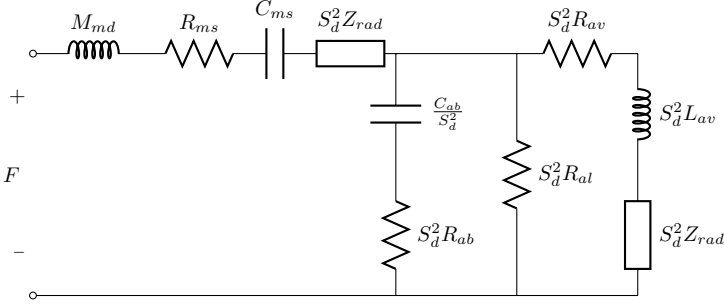


Figure 4.7: Mechanical-Acoustic Circuit Model

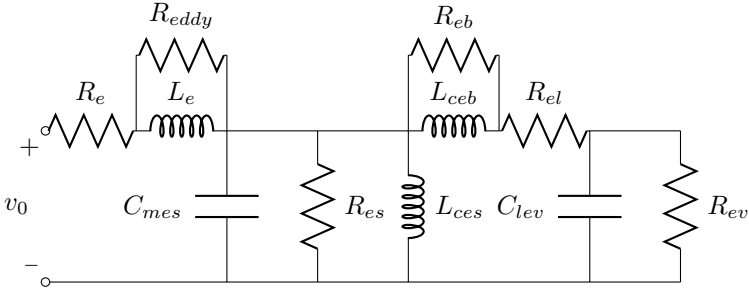


Figure 4.8: Electro-Mechanical-Acoustic Circuit Model

4.4 Combined Model

In this section, we will combine our models into a single model, then show how measurements can extract values for each of the components.

First, we combine the acoustic model with the mechanical using Equations 4.10 and 4.11 to generate Figure 4.7.

Next, we remember Equation 4.9 to convert from mechanical impedances to electrical $Z_e = (B\ell)^2 Z_m^{-1}$. That means we have to find the dual of Figure 4.7 and place that circuit in Figure 4.2. The resulting equivalent circuit model is presented in Figure 4.8; variables are defined in Tables 4.2, 4.3, and 4.4.

Variable	Definition	Description
Z_a	$\frac{p}{Q}$	Acoustic impedance
S_d		Speaker driver area
R_{rad}	$\frac{\omega^2 \rho}{2\pi c}$	Acoustic impedance of monopole radiation in to a hemisphere
L_{rad}	$\frac{\rho a}{A_v}$	Acoustic inductance of monopole radiation in to a hemisphere
C_{ab}	$\frac{V}{\rho c^2}$	Acoustic compliance from compression of air in a box with volume V
R_{ab}		Acoustic resistance of acoustic dampening from fill material in box
R_{al}	$\frac{\mu l}{\kappa A}$	Acoustic resistance from air leakage out of the enclosure with surface area A and wall thickness l
L_{av}	$\frac{\rho l_v}{A_v}$	Acoustic Inductance from a mass of air flowing through a vent/port of area A_v and length l_v
R_{av}	$\frac{\mu l_v}{\kappa A_v}$	Acoustic resistance of vent/port acoustic radiation and of viscous air flow through a vent/port of area A_v and length l_v

Table 4.2: Acoustic Variable Definitions

Variable	Definition	Description
Z_m	$\frac{F}{v} = S_d^2 Z_a$	Mechanical impedance
M_{md}		Mass of the diaphragm and coil
M_{ms}	$M_{md} + S_d^2 L_{rad}$	Mass of the diaphragm, coil, and acoustic load
R_{ms}		Suspension mechanical dampening
C_{ms}		Suspension mechanical compliance
V_{as}	$\rho c^2 S_d^2 C_{ms}$	Commonly used term for mechanical compliance as the volume of air with equivalent mechanical compliance C_{ms}
$B\ell$		Voice coil magnet strength

Table 4.3: Mechanical Variable Definitions

Figure 4.8 describes a vented box, but can easily be modified for sealed box or open baffle by the conversion described in 4.5.

In all cases, several simple conclusions can be drawn. To maximize output efficiency, make all non-radiative losses small: fully seal the box $R_{el} = 0$; make the port area as large as possible so R_{ev} is limited to acoustic radiation; choose efficient drivers (low eddy current effects, high- Q drivers); and use as little filler material as necessary R_{eb} . The guidelines lead to the common simplified model as seen in Figure 4.9. Additionally, port radiation through R_{ev} is relatively low, therefore R_{ev} is large and removed from the model. Port volume velocity can still be found since it is proportional to the electrical potential over C_{lev}

Variable	Definition	Description
Z_e	$\frac{(B\ell)^2}{Z_m}$	Electric Impedance
R_e		Electrical resistance of the voice coil
L_e		Electrical inductance of the voice coil
R_{eddy}		Losses due to inductive currents near voice coil
C_{es}	$\frac{M_{ms}}{(B\ell)^2}$	Equivalent electrical capacitance from diaphragm and voice coil mass
R_{es}	$\frac{(B\ell)^2}{R_{ms} + S_d^2 R_{rad}}$	Equiv. electrical resistance of suspension mechanical dampening and front acoustic radiation
L_{ces}	$(B\ell)^2 C_{ms}$	Equiv. electrical inductance of the suspension's mechanical compliance
L_{ceb}	$\frac{(B\ell)^2}{S_d^2} \frac{V}{\rho c^2}$	Equiv. electrical inductance from air compression in a box with volume V
R_{eb}	$\frac{(B\ell)^2}{S_d^2 R_{ab}}$	Equiv. electrical resistance of fill material in box
R_{el}	$\frac{(B\ell)^2}{S_d^2} \frac{\kappa A}{\mu l}$	Equiv. electrical resistance of air leakage in the enclosure with surface area A and thickness l
C_{lev}	$\frac{S_d^2}{(B\ell)^2} \frac{\rho(l + \frac{a_v}{2})}{A}$	Equiv. electrical capacitance from a vent air mass (area A , length l) adding a length of $1/2$ radius ($a/2$) from vent radiation
R_{ev}	$\frac{(B\ell)^2}{S_d^2 (\frac{\mu l}{\kappa A} + R_{rad})}$	Equiv. electrical resistance of vent acoustic radiation and of viscous air flow through a vent (area A , length l)
R_{er}	$\frac{(B\ell)^2}{S_d^2} \frac{2\pi c}{\omega^2 \rho}$	Equiv. electrical resistance of acoustic radiation

Table 4.4: Electric Variable Definitions

Variable	Sealed	Open Box
L_{ceb}	Yes	No (short)
R_{eb}	Yes	No (open)
R_{el}	Yes	No (open)
C_{lev}	No (open)	No (open)
R_{ev}	No (open)	No (open)

Table 4.5: Vented Box Model conversion to sealed and open baffle

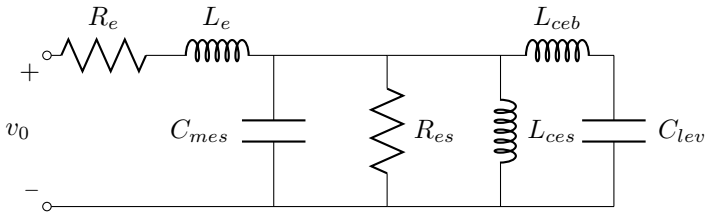


Figure 4.9: Simplified Electrical Mechanical Acoustic Circuit Model

Chapter 5

Loudspeaker Box Design

Speaker in Free Air: We can use our understanding and model in Figure 4.9 to come up with the why and how we need speaker enclosures. Consider, at first, a speaker driver sitting in free air in Figure 5.1. The right two resistors have the same value and represent acoustic power transmitted as sound. Although they are much larger than R_{es} , they are included to show the back and rear polarities are opposite. As such, total output power is *zero*. Not exactly the world's best speakers!

Still, there is some insight to be gained about system performance. Prior ubiquitous computing and measurement techniques,

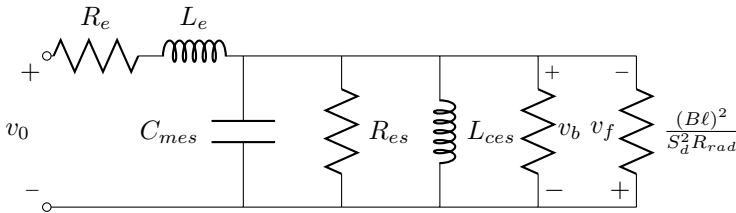


Figure 5.1: Simplified Model of Speaker Driver in Free Air

the easiest responses to measure were the peak frequency response and bandwidth, simply by measuring acoustic audio output versus input frequency. We can find the expressions for resonance frequency f_s and $f_s/\Delta f = Q$ of power dissipated in the mechanical resonator.

$$\langle P \rangle = \frac{|F_R|^2}{2R} \quad (5.1)$$

$$F_R = \frac{R}{i\omega M_{ms} + R_{ms} + \frac{1}{i\omega C_{ms}}} \quad (5.2)$$

$$\omega_s M_{ms} - \frac{1}{\omega_s C_{ms}} = 0 \quad (5.3)$$

$$\omega_s = \frac{1}{\sqrt{M_{ms} C_{ms}}} \quad (5.4)$$

$$f_s = \frac{1}{2\pi \sqrt{M_{ms} C_{ms}}} \quad (5.5)$$

Q can also be computed as $Q = 2\pi \times \frac{W_{store}}{W_{loss/cycle}} = \omega_s \frac{W}{P}$ (ratio of energy stored in resonator to $2\pi \times$ energy loss per cycle). At resonance, the total energy stored is the same as the peak energy stored in either the capacitor or inductor ($\frac{1}{2}LI_p^2$ or $\frac{1}{2}CV_p^2$), and time average power loss is $\frac{1}{2}RI_p^2$ or $\frac{1}{2}\frac{V_p^2}{R}$. To solve for Q , use the component that corresponds to whether R sees the same I or V as the resonator (i.e., in series or parallel, respectively). There are two reasons for energy loss: mechanical (R_{es}) and electrical (R_e). Commonly these are separated independently, then combined. This was done because R_e was easy to measure with a multimeter, and therefore measuring the combined Q_t while knowing Q_e gave people a way to indirectly measure R_{es} :

$$Q_{ms} = \omega_s \frac{v^2 M_{ms}}{v^2 R_{ms}} = \frac{2\pi f_s M_{ms}}{R_{ms}} = 2\pi f_s R_{es} C_{es} \quad (5.6)$$

Now we can find the expression for electrical power dissipated from the mechanical resonance, thus only considering electrical losses. Since R_e and C_{mes} see the same I_{peak} :

$$Q_{es} = \omega_s \frac{I^2 C_{es}}{I^2 / R_e} = 2\pi f_s R_e C_{es} = \frac{2\pi f_s R_e M_{ms}}{(B\ell)^2} \quad (5.7)$$

Since Q is energy stored per power dissipated, if a resonator has two ways of dissipating energy but one way of storing it, then the combined Q can be found:

$$Q_{ts} = \frac{\omega W_{store}}{P_e + P_m} = \left(\frac{P_e}{\omega W_{store}} + \frac{P_m}{\omega W_{store}} \right)^{-1} = \frac{Q_{es} Q_{ms}}{Q_{es} + Q_{ms}} \quad (5.8)$$

5.1 Speaker with an Infinite Baffle

The problem with our free space speaker was the interference of the sound from the front and back of the speaker driver. We can block the sound from the back of the driver by walling off the space between the front and back of the driver. Figure 5.1 stays the same, but our output acoustic power is solely from the front of the driver. We can compute the output acoustic power of this system as a function of frequency:

$$P_a = \frac{|v_f|^2}{2R_{er}} \quad (5.9)$$

$$v_f = v_0 \times \frac{\hat{Z}_e}{R_e + i\omega L_e + \hat{Z}_e} \quad (5.10)$$

$$P_a = \frac{|v_o|^2 |\hat{Z}_e|^2}{2R_{er} |R_e + i\omega L_e + \hat{Z}_e|^2} \quad (5.11)$$

We then do something that may appear silly, but will help us out a lot later - we multiply the right term by $\left[\left(\frac{R_e C_{es}}{R_e C_{es}} \right)^2 \left(\frac{-i^2}{-i^2} \right) \right]$ and bring ω^2 into the right term:

$$P_a = \frac{|v_o|^2 S_d^2 \omega^2 \rho}{4\pi c (B\ell)^2 R_e^2 C_{es}^2} \left| \frac{-i R_e C_{es} \omega \hat{Z}_e}{R_e + i\omega L_e + \hat{Z}_e} \right|^2 \quad (5.12)$$

$$P_a(\omega) = \frac{|v_o|^2 S_d^2 \omega^2 \rho}{4\pi c (B\ell)^2 R_e^2 C_{es}^2} |\hat{H}(\omega)|^2 \quad (5.13)$$

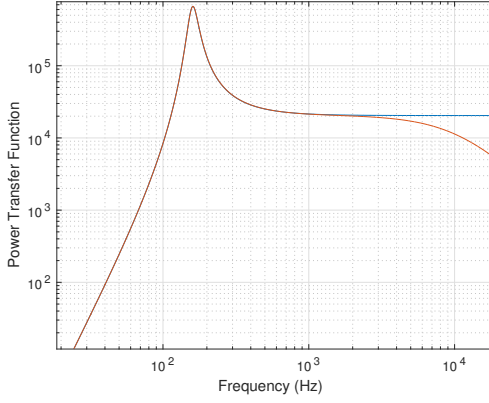


Figure 5.2: Infinite Baffle Power Transfer Function for $R_e = 7$. $C_{es} = 1e - 3$, $L_{es} = 1e - 3$, $R_{es} = 30$. Red curve: $L_e = 1e - 4$, Blue curve: $L_e = 0$

The term on the right of Equation 5.13 is the power transfer function $\left| \hat{H}(\omega) \right|^2$. The form of the function is seen in Figure 5.2. It peaks at f_s , and in the presence of L_e (red) decreases output at higher frequencies. However, to gain some more insight, we will ignore the effects of L_e .

Looking into the power transfer function:

$$G(\omega) = \left| \hat{H}(\omega) \right|^2 = \left| \frac{-iR_e C_{es} \omega \hat{Z}_e}{R_e + \hat{Z}_e} \right|^2 \quad (5.14)$$

$$\hat{H}(\omega) = \frac{\omega^2}{-\omega^2 C_{es} L_{es} + i\omega L_{es} (R_e^{-1} + R_{es}^{-1}) + 1} \quad (5.15)$$

We can recognize $\omega_s = \frac{1}{\sqrt{C_{es} L_{es}}}$ so we set the characteristic frequency $\omega_c = \omega_s$, and for clarity define $R_t = \frac{R_e R_{es}}{R_e + R_{es}}$:

$$\hat{H}(\omega) = \frac{(\omega/\omega_c)^2}{-\frac{\omega^2}{\omega_c^2} + \frac{i\omega}{\omega_c} \frac{1}{R_t} \sqrt{\frac{L_{es}}{C_{es}}} + 1} \quad (5.16)$$

And, in the great reveal, we examine Equation 5.8 to find Q_{ts} in terms of R_e , R_{es} , L_{es} , and C_{es} :

$$Q_{ts} = \frac{R_e R_{es}}{R_e + R_{es}} \sqrt{\frac{C_{es}}{L_{es}}} \quad (5.17)$$

$$\hat{H}(\omega) = \frac{(\omega/\omega_c)^2}{-\frac{\omega^2}{\omega_c^2} + \frac{i\omega}{\omega_c} \frac{1}{Q_{ts}} + 1} \quad (5.18)$$

Which is the form of a second-order high-pass filter! Can we use this to turn the system in to a Butterworth filter with a flat pass-band and phase response? For a second order Butterworth filter:

$$G(\omega) = \frac{(\omega/\omega_c)^4}{1 + \left(\frac{\omega}{\omega_c}\right)^4} = \left| \frac{(\omega/\omega_c)^2}{-\left(\frac{\omega}{\omega_c}\right)^2 + \sqrt{2} \frac{i\omega}{\omega_c} + 1} \right|^2 \quad (5.19)$$

So if we can get $Q_{ts}^{-1} = \frac{L_{es}}{R_t \sqrt{C_{es} L_{es}}} = \sqrt{2}$, our speaker will have a flat pass band and phase response! How can we do that? Well, if you put the back of the speaker in a sealed and enclosed area, there will be a L_{ceb} in parallel to L_{es} from the compliance (“springy-ness”) of the air in the box – we can use that to make our Butterworth filter by choosing the correct box volume!

5.2 Sealed Box Enclosure

We’re now able to attempt optimizing our sealed box replacing $L_{es} \rightarrow L_t = (L_{es}^{-1} + L_{ceb}^{-1})^{-1}$ in Equation 5.16 and set it to the 2nd order Butterworth condition:

$$\frac{1}{R_t} \sqrt{\frac{L_t}{C_{es}}} = \sqrt{2} \quad (5.20)$$

$$L_t = 2R_t^2 C_{es} \quad (5.21)$$

$$\frac{L_{es} L_{ceb}}{L_{es} + L_{ceb}} = 2R_t^2 C_{es} \quad (5.22)$$

$$L_{ceb} = \frac{2R_t^2 C_{es} L_{es}}{L_{es} - 2R_t^2 C_{es}} \quad (5.23)$$

$$V_b = \frac{\rho c^2 S_d^2}{(B\ell)^2} \frac{2R_t^2 C_{es} L_{es}}{L_{es} - 2R_t^2 C_{es}} \quad (5.24)$$

A perhaps more clear expression is:

$$\frac{1}{L_{ceb}} = \frac{1}{2R_t^2 C_{es}} - \frac{1}{L_{es}} \quad (5.25)$$

L_{es} is commonly given in acoustic units of:

$$V_{as} = \rho c^2 S_d^2 L_{es} / (B\ell)^2 \quad (5.26)$$

$$= \rho c^2 S_d^2 L_{ms} \quad (5.27)$$

Converting the remaining terms to acoustic units yields:

$$\frac{\rho c^2 S_d^2}{V_b (B\ell)^2} = \frac{1}{2C_{ms} Q_{ts}^2 (B\ell)^2} - \frac{\rho c^2 S_d^2}{V_{as} (B\ell)^2} \quad (5.28)$$

$$\frac{\rho c^2 S_d^2}{V_b} = \frac{\rho c^2 S_d^2}{2V_{as} Q_{ts}^2} - \frac{\rho c^2 S_d^2}{V_{as}} \quad (5.29)$$

$$\frac{1}{V_b} = \frac{1}{2V_{as} Q_{ts}^2} - \frac{1}{V_{as}} \quad (5.30)$$

$$V_b = V_{as} \frac{2Q_{ts}^2}{1 - 2Q_{ts}^2} \quad (5.31)$$


And generally, you can see the number 2 comes from $1/Q_t^2$ where Q_t is the desired total system Q , therefore

$$V_b = V_{as} \frac{(Q_{ts}/Q_t)^2}{1 - (Q_{ts}/Q_t)^2} \quad (5.32)$$

Which is commonly described as the *compression ratio* (α):

$$\alpha = \frac{V_{as}}{V_b} = \frac{1 - (Q_{ts}/Q_t)^2}{(Q_{ts}/Q_t)^2} \quad (5.33)$$

That's it! Some important notes: sealed boxes only work if the current Q_{ts} is less than the desired Q_t (i.e., $Q_{ts} < Q_t$). For a 2nd order Butterworth filter, $Q_t \approx 0.7$, so $Q_{ts} > 0.7$ to achieve B2 alignment. Also, it is possible to use other 2nd order filters to

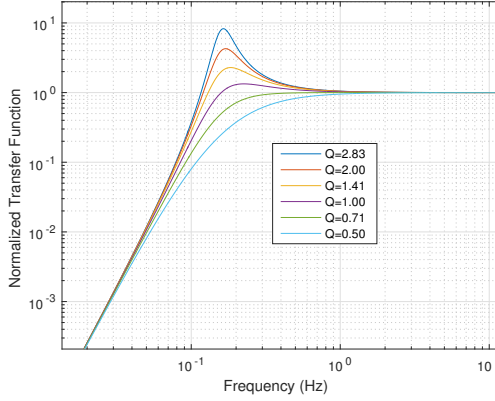Figure 5.3: Normalized Acoustic Power in a Sealed Box Versus Q

obtain specific design criteria by choosing a desired that is not B2 alignment. If $Q_t \neq 1/\sqrt{2}$, one can tune low-frequency response and peak at ω_s). The effect of choice of Q is depicted in Figure 5.3.

In this example, we only touched L , but it is also possible to similarly affect R_t by adding an additional electric resistance in parallel with (or acoustic resistance in series with) the box compliance. That is the equivalent of filling the box with an acoustically absorbing material. This does two things: it properly adds compliance while keeping the speaker compact and it does not negatively effect efficiency, as seen in the previous discussion.

System resonance and roll-off frequency f_3 (corresponding to where response is 1/2 of the peak value, or -3 dB, which describes the minimum frequency output of the system) will be changed. The new characteristic frequency ω_c and f_3 can be found with the addition of box compliance C_{mb} :

$$\omega_c = \left(\sqrt{\frac{C_{ms}C_{mb}}{C_{ms} + C_{mb}}} M_{ms} \right)^{-1} = \omega_s \sqrt{\frac{C_{ms}}{C_{mb}}} + 1 = \omega_s \sqrt{\frac{V_{as}}{V_b}} + 1 \quad (5.34)$$

and to find ω_3 :

$$G(\omega_3) = 1/2 \quad (5.35)$$

$$\frac{(\omega_3/\omega_c)^4}{\left[-\left(\frac{\omega_3}{\omega_c}\right)^2 + \frac{1}{Q_t} \frac{i\omega_3}{\omega_c} + 1\right]^2} = \frac{1}{2} \quad (5.36)$$

$$\left(\frac{\omega_3}{\omega_c}\right)^4 + \left(2 - \frac{1}{Q_t^2}\right) \left(\frac{\omega_3}{\omega_c}\right)^2 - 1 = 0 \quad (5.37)$$

$$\omega_3 = \omega_c \left[\frac{\frac{1}{Q_t^2} - 2 \pm \sqrt{\left(2 - \frac{1}{Q_t^2}\right)^2 + 4}}{2} \right]^{1/2} \quad (5.38)$$

Absolute values and \pm is from finding the roots of a polynomial of order ω_3^4 , and allows for both peaked and low-pass responses. It's important to see that and ω_3 is a minimum when $Q_t = 1/\sqrt{2}$ – the B2 alignment!

Therefore, for a B2 closed-box alignment:

$$\alpha = \frac{1 - 2Q_{ts}^2}{2Q_{ts}^2} \quad \omega_3 = \omega_c = \omega_s \sqrt{\alpha + 1} \quad (5.39)$$

Finally, actual box dimensions can be chosen now that we know V_b . The most important thing is to choose irrational numbers to prevent standing waves. For example, the golden ratio (0.6 : 1 : 1.6) or $2^{-1/2} : 2^0 : 2^{1/2}$ are sometimes used.

5.3 Vented/Ported/Bass-Reflex Enclosures

Similar to the sealed box case, we can find the output power of a vented enclosure as seen in Figure 4.4 and 4.9. Acoustic output is from the sum of two volume velocities corresponding to front and back radiation (Q_f and Q_b). The total volume velocity is thus $Q_f - Q_b$, which in electrical units corresponds to $v_s - v_{C_{Lev}}$. In electrical units, the acoustic output power can be calculated as:

$$\begin{aligned}
\langle P_{ao} \rangle &= \frac{|v_s - v_{C_{lev}}|^2}{2R_{er}} = \frac{|v_{L_{ceb}}|^2}{2R_{er}} = \frac{S_d^2 \omega^2 \rho |v_{L_{ceb}}|^2}{4\pi c (B\ell)^2 R_e^2 C_{es}^2} \\
&= \frac{S_d^2 \rho}{4\pi c (B\ell)^2 R_e^2 C_{es}^2} |\hat{H}_\omega|^2
\end{aligned} \tag{5.40}$$

and represents the fact that the front and back mechanical motions are 180° out of phase.

$$\hat{H}_\omega = (-iR_e C_{es} \omega) v_{L_{ceb}} = \frac{-iC_{ev} L_{ceb} R_{es} L_{es} \omega^4}{A_4' \omega^4 - iA_3' \omega^3 - A_2' \omega^2 + iA_1' \omega + A_0'} \tag{5.41}$$

$$A_4' = C_{lev} L_{ceb} R_e R_{es} C_{es} L_{es} \tag{5.42}$$

$$A_3' = C_{lev} L_{ceb} R_{es} L_{es} + C_{lev} L_{ceb} R_e L_{es} \tag{5.43}$$

$$A_2' = R_e R_{es} C_{es} L_{es} + C_{lev} R_e R_{es} L_{es} + C_v L_{ceb} R_e R_{es} \tag{5.44}$$

$$A_1' = R_{es} L_{es} + R_e L_{es} \tag{5.45}$$

$$A_0' = R_e R_{es} \tag{5.46}$$

normalizing by A_0' and defining $R_t = \frac{R_e R_{es}}{R_{es} + R_e}$, $Q_{ts} = R_t \sqrt{\frac{C_{es}}{L_{es}}}$, $\omega_s = \frac{1}{\sqrt{C_{es} L_{es}}}$, and $\omega_b = \frac{1}{\sqrt{C_{lev} L_{ceb}}}$

$$\hat{H}(\omega) = (-iR_e C_{es} \omega) \times v_{L_{ceb}} = \frac{(-iR_e C_{es})(-iC_{ev} L_{ceb} L_{es}) \omega^4 / R_e}{A_4 \omega^4 - iA_3 \omega^3 - A_2 \omega^2 + iA_1 \omega + 1} \tag{5.47}$$

$$\hat{H}(\omega) = \frac{-i\omega_s}{Q_{es}} \frac{\omega^4 / \omega_b^2 \omega_s^2}{A_4 \omega^4 - iA_3 \omega^3 - A_2 \omega^2 + iA_1 \omega + 1} \tag{5.48}$$

$$A_4 = C_{lev} L_{ceb} C_{es} L_{es} = \frac{1}{\omega_b^2 \omega_s^2} \tag{5.49}$$

$$A_3 = \frac{C_{lev}L_{ceb}L_{es}}{R_t} = \frac{1}{\omega_b^2\omega_s Q_{ts}} \quad (5.50)$$

$$A_2 = C_{es}L_{es} + C_{lev}L_{es} + C_{lev}L_{ceb} = \frac{1}{\omega_s^2} + \frac{1}{\omega_b^2} + \frac{L_{es}}{L_{eb}} \frac{1}{\omega_b^2} \quad (5.51)$$

$$A_1 = \frac{L_{es}}{R_t} = \frac{1}{Q_{ts}\omega_s} \quad (5.52)$$

This can be seen as a 4th order filter, we just have to choose our the variables to properly “align” with the audio response we want. Thiele observed that for drivers with $Q_{ts} = 0.383$, a “perfect” fourth order Butterworth filter can be made if ω_b and V_b are chosen properly; when $Q_{ts} < 0.383$, you can get a “Quasi-Butterworth Third Order” alignment; and for drivers $Q_{ts} > 0.383$ a “Fourth Order Chebyshev” alignment is suitable. Both Thiele and Small created tables and graphical tools to aid design. Modern computers give us an alternative tool which is especially helpful for two- or three-way speakers (multiple drivers in the same box). For completeness, we will find the analytical expressions then describe how computers can be used.

5.3.1 Fourth Order Butterworth Filter (B4)

$$Q_{ts} = 0.383$$

A fourth order Butterworth filter produces a power response of the form:

$$\left| \hat{H}(\omega) \right|^2 \propto \frac{(\omega/\omega_c)^8}{1 + \left(\frac{\omega}{\omega_c} \right)^8} \quad (5.53)$$

$$\begin{aligned} \hat{H}(\omega) &= \frac{\left(\frac{\omega}{\omega_c} \right)^4}{\left(\frac{\omega}{\omega_c} \right)^4 - i2.6132 \left(\frac{\omega}{\omega_c} \right)^3 - 3.414 \left(\frac{\omega}{\omega_c} \right)^2 + i2.613 \left(\frac{\omega}{\omega_c} \right) + 1} \\ &= \frac{\left(\frac{\omega}{\omega_c} \right)^4}{\left(\frac{\omega}{\omega_c} \right)^4 - iA_3 \left(\frac{\omega}{\omega_c} \right)^3 - A_2 \left(\frac{\omega}{\omega_c} \right)^2 + iA_1 \left(\frac{\omega}{\omega_c} \right) + 1} \end{aligned} \quad (5.54)$$

We can now use this to design the box by using Equation 5.53 to generate the following relationships:

$$\omega_c = \sqrt{\omega_b \omega_s} = \omega_3 \quad (5.55)$$

$$A_1/\omega_c = 1/Q_{ts}\omega_s \quad (5.56)$$

$$A_2/\omega_c^2 = 1/\omega_s^2 + 1\omega_b^2 + (L_{es}/L_{eb})(1/\omega_b^2) \quad (5.57)$$

$$A_3/\omega_c^3 = 1/\omega_b^2\omega_s Q_{ts} \quad (5.58)$$

where ω_c is the characteristic frequency of the box, which in the case of the B4 filter is also the frequency where Equation 5.53 is 1/2 of the maximum value (i.e., 3dB lower, ω_3). This gives us our dimensions for the box!

$$\frac{V_{as}}{V_b} = \frac{A_1 A_2 A_3 - A_1^2 - A_3^2}{A_3^2} = \alpha \quad (5.59)$$

$$\frac{\omega_b}{\omega_s} = \frac{A_1}{A_3} = h \quad (5.60)$$

$$\omega_b = (C_{ev} L_{eb})^{-1/2} = \sqrt{\frac{c^2 A_v}{V_b l_v}} = h \omega_s \quad (5.61)$$

$$\frac{l_v}{A_v} = \frac{\alpha c^2}{V_{as} h^2 \omega_s^2} \quad (5.62)$$

$$Q_{ts} = \frac{1}{\sqrt{A_1 A_3}} \quad (5.63)$$

For a B4 alignment, yields:

$$\omega_c = \omega_s = \omega_b \quad (5.64)$$

$$Q_t = 0.383 \quad (5.65)$$

$$\frac{L_{es}}{L_{eb}} = \frac{V_{as}}{V_{ab}} = 1.414 \quad (5.66)$$

which allows us to write $\hat{H}(\omega)$ as:

$$\hat{H}(\omega) = \frac{\left(\frac{\omega}{\omega_c}\right)^4}{\left(\frac{\omega}{\omega_c}\right)^4 - i \frac{1}{Q_t} \left(\frac{\omega}{\omega_c}\right)^3 - \left(2 + \frac{L_{es}}{L_{eb}}\right) \left(\frac{\omega}{\omega_c}\right)^2 + i \frac{1}{Q_t} \frac{\omega}{\omega_c} + 1} \quad (5.67)$$

To make a forth order Butterworth box:

1. Make the box volume is: $V_b = \frac{1}{\sqrt{2}} V_{as}$
2. The vent dimensions are: $\frac{A_v}{l_v} = \frac{\omega_s^2 V_{as}}{c^2 \sqrt{2}}$. This is found from $\omega_b^2 = \omega_s^2 = \frac{1}{C_{ev} L_{eb}} = \frac{1}{V_b l_v / (c^2 A_v)} = \frac{\sqrt{2} c^2 A_v}{V_{as} l_v}$
3. Q_{ts} will need to be tuned by placing a resistor in series with the speaker, thus effectively increasing R_e . Therefore, in this alignment (i.e., this choice of filter parameters), only $Q_{ts} > 0.383$ are easily implemented. However, this technique of using a resistor to decrease Q_{es} is rarely¹ done since it also reduces output power when similar performance can be found with the Chebyshev (C4) alignment described below.

The fourth order Butterworth (i.e., “B4”) filter only really is suitable for $Q_{ts} = 0.383$ drivers. Other alignments make vented boxes for other Q_{ts} possible.

5.3.2 Fourth Order Chebyshev (C4)

$$Q_{ts} > 0.383$$

Thiele uses the fact that Chebyshev filters are Butterworth filters where the real part of the Butterworth filter poles (i.e., the roots of the denominator) are multiplied by the same factor k . For example, in a B4 filter (with $s = i\omega/\omega_c$), the poles are the roots of the denominator of the low-pass transfer function:

$$\hat{H}(s) = \frac{1}{s^4 + 2.6132s^3 + 3.414s^2 + 2.613s + 1} \quad (5.68)$$

$$s = \{-0.3827 \pm 0.9239i; -0.9239 \pm 0.3827i\} \quad (5.69)$$

We can therefore convert the B4 filter to a Chebyshev filter form by multiplying the real part of each of the roots by k which gives us a low-pass Chebyshev filter of the form:

$$\hat{H}(s) = \prod_i \frac{-1}{s/p_i - 1} = \prod_i \frac{-p_i}{s - p_i} \quad (5.70)$$

¹rarely=never

where i is the index of the i th pole.

The low-pass Chebyshev filter that has the same roots described in Equation 5.69 is:

$$\hat{H}(s) = \frac{a_4}{s^4 + a_1 s^3 + a_2 s^2 + a_3 s + a_4} \quad (5.71)$$

where:

$$\begin{aligned} a_1 &= 2.6131k \\ a_2 &= 2.4143k^2 + 1 \\ a_3 &= 0.9239k^3 + 1.6892k \\ a_4 &= 0.1250k^4 + 0.7500k^2 + 0.1250 \end{aligned} \quad (5.72)$$

Transforming Equation 5.71 to a high-pass filter means changing all $s \rightarrow s^{-1}$:

$$\hat{H}(s) = \frac{a_4 s^4}{1 + a_1 s + a_2 s^2 + a_3 s^3 + a_4 s^4} \quad (5.73)$$

The frequency response ($s = i\omega/\omega_c$) is therefore:

$$\hat{H}(s) = \frac{a_4 \left(\frac{\omega}{\omega_c}\right)^4}{1 + ia_1 \left(\frac{\omega}{\omega_c}\right) - a_2 \left(\frac{\omega}{\omega_c}\right)^2 - ia_3 \left(\frac{\omega}{\omega_c}\right)^3 + a_4 \left(\frac{\omega}{\omega_c}\right)^4} \quad (5.74)$$

and defining a new $\omega'_c = \omega_c/a_4^{1/4}$:

$$\hat{H}(s) = \frac{\left(\frac{\omega}{\omega'_c}\right)^4}{1 + i\frac{a_1}{a_4^{1/4}} \left(\frac{\omega}{\omega'_c}\right) - \frac{a_2}{a_4^{1/2}} \left(\frac{\omega}{\omega'_c}\right)^2 - i\frac{a_3}{a_4^{3/4}} \left(\frac{\omega}{\omega'_c}\right)^3 + \left(\frac{\omega}{\omega'_c}\right)^4} \quad (5.75)$$

$$= \frac{\left(\frac{\omega}{\omega'_c}\right)^4}{1 + iA_1 \left(\frac{\omega}{\omega'_c}\right) - A_2 \left(\frac{\omega}{\omega'_c}\right)^2 - iA_3 \left(\frac{\omega}{\omega'_c}\right)^3 + \left(\frac{\omega}{\omega'_c}\right)^4} \quad (5.76)$$

where:

$$\omega'_c = \sqrt{\omega_b \omega_s} \quad (5.77)$$

$$A_1 = \frac{2.6131k}{(0.1250k^4 + 0.7500k^2 + 0.1250)^{1/4}} \quad (5.78)$$

$$A_2 = \frac{2.4143k^2 + 1}{(0.1250k^4 + 0.7500k^2 + 0.1250)^{2/4}} \quad (5.79)$$

$$A_3 = \frac{0.9239k^3 + 1.6892k}{(0.1250k^4 + 0.7500k^2 + 0.1250)^{3/4}} \quad (5.80)$$

When $k = 1$, you can see that the A_1 , A_2 , A_3 are the same as the B4 coefficient alignments when $k = 1$.

We can now find the dimensions and performance specifications for our speaker! First we need to find what k corresponds to our speaker. This can be found from our driver's specified Q_{ts} and solving for k :

$$Q_{ts} = \frac{1}{\sqrt{A_1 A_3}} \quad (5.81)$$

Next we find the volume of the box from $V_{as}/V_b = L_{es}/L_{eb}$:

$$\frac{V_{as}}{V_b} = \frac{A_1 A_2 A_3 - A_1^2 - A_3^2}{A_3^2} = \alpha \quad (5.82)$$

We find the required ω_b (i.e., the dimensions of the port as a function of box volume) from:

$$\frac{\omega_b}{\omega_s} = \frac{A_1}{A_3} = h \quad (5.83)$$

and the characteristic frequency frequency from:

$$\omega'_c = \sqrt{\omega_b \omega_s} = \omega_s \sqrt{h} \quad (5.84)$$

Finally, the cut-off frequency (when 3dB lower than the value at high frequencies) is given by solving for when the power spectrum (i.e., the square of the magnitude of Equation 5.76) is 1/2 of the high-frequency value.

$$\hat{H}(\omega) = \frac{\left(\frac{\omega}{\omega'_c}\right)^4}{1 + iA_1\left(\frac{\omega}{\omega'_c}\right) - A_2\left(\frac{\omega}{\omega'_c}\right)^2 - iA_3\left(\frac{\omega}{\omega'_c}\right)^3 + \left(\frac{\omega}{\omega'_c}\right)^4} \quad (5.85)$$

$$\left|\hat{H}(\omega_3)\right|^2 = \frac{\left(\frac{\omega_3}{\omega'_c}\right)^8}{1 + B_1\left(\frac{\omega_3}{\omega'_c}\right)^2 + B_2\left(\frac{\omega_3}{\omega'_c}\right)^4 + B_3\left(\frac{\omega_3}{\omega'_c}\right)^6 + \left(\frac{\omega_3}{\omega'_c}\right)^8} = \frac{1}{2} \quad (5.86)$$

$$B_1 = A_1^2 - 2A_2 \quad (5.87)$$

$$B_2 = 2 + A_2^2 - 2A_1A_3 \quad (5.88)$$

$$B_3 = A_3^2 - 2A_2 \quad (5.89)$$

So to find ω_3 you first need to find the roots of:

$$\frac{1}{\left(\frac{\omega'_c}{\omega_3}\right)^8 + B_1\left(\frac{\omega'_c}{\omega_3}\right)^6 + B_2\left(\frac{\omega'_c}{\omega_3}\right)^4 + B_3\left(\frac{\omega'_c}{\omega_3}\right)^2 + 1} = \frac{1}{2} \quad (5.90)$$

$$\left(\frac{\omega'_c}{\omega_3}\right)^8 + B_1\left(\frac{\omega'_c}{\omega_3}\right)^6 + B_2\left(\frac{\omega'_c}{\omega_3}\right)^4 + B_3\left(\frac{\omega'_c}{\omega_3}\right)^2 - 1 = 0 \quad (5.91)$$

$$d^4 - B_3d^3 - B_2d^2 - B_1d - 1 = 0 \quad (5.92)$$

where $d = (\omega_3/\omega'_c)^2$. Taking the largest real root of d yields:

$$\frac{\omega_3}{\omega_s} = \sqrt{dh} \quad (5.93)$$

5.3.3 Third Order Quasi-Butterworth (QB3)

$$Q_{ts} < 0.383$$

When $Q_{ts} < 0.38$, you can use a “Third Order Quasi-Butterworth” alignment. This filter is described by the transfer function:

$$\left|\hat{H}(s)\right|^2 = \frac{(\omega/\omega_c)^8}{(\omega/\omega_c)^8 + B^2(\omega/\omega_c)^2 + 1} \quad (5.94)$$

Which reduces to a fourth order Butterworth filter $B = 0$. We can see what generic filter behaves like this QB3 filter by comparing a generic fourth-order filter with the form:

$$\hat{H}(\omega) = \frac{(\omega/\omega_c)^4}{(\omega/\omega_c)^4 - iA_3(\omega/\omega_c)^3 - A_2(\omega/\omega_c)^2 + iA_1(\omega/\omega_c) + 1} \quad (5.95)$$

therefore, to be a QB3 filter:

$$A_3^2 - 2A_2 = 0 \quad (5.96)$$

$$2 + A_2^2 - 2A_1A_3 = 0 \quad (5.97)$$

$$A_1^2 - 2A_2 = B^2 \quad (5.98)$$

therefore:

$$A_3 = \sqrt{2A_2} \quad (5.99)$$

$$A_1 = \frac{2 + A_2^2}{2A_3} = \frac{2 + A_2^2}{2\sqrt{2A_2}} \quad (5.100)$$

Using equations 5.59–5.63 with 5.96–5.98 yields:

$$\frac{w_b}{w_s} = \frac{1}{Q_{ts}\sqrt{8 - 8Q_{ts}^2}} = h \quad (5.101)$$

$$\frac{V_{as}}{V_b} = \frac{A_1A_2A_3 - A_1^2 - A_3^2}{A_3^2} = \alpha \quad (5.102)$$

$$\omega_c = \sqrt{\omega_s\omega_b} \quad (5.103)$$

$$A_2 = \frac{1}{2Q_{ts}^2h} = \sqrt{2(1/Q_{ts}^2 - 1)} \quad (5.104)$$

from which A_1 , A_3 , and B can be calculated, and which will give us the box dimensions.

We also can model the box's performance. The low frequency cut-off ω_3 (i.e., 3 dB down from the high-frequency response) can be found from making Equation 5.104 equal $1/2$ and solving for ω/ω_c . Then using the relationship that $\omega_3\sqrt{h}/\omega_c = \omega_3/\omega_s$, we can find the normalized cut-off frequency:

$$\frac{1}{1 + B^2 \left(\frac{\omega_c}{\omega_3}\right)^6 + \left(\frac{\omega_c}{\omega_3}\right)^8} = \frac{1}{2} \quad (5.105)$$

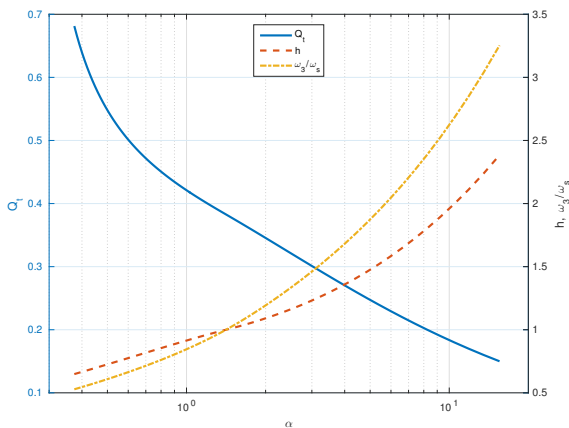


Figure 5.4: Graphical solution for finding compression ratio α , normalized box and cut-off frequencies (h and ω_3) for a given Q_t

$$\left(\frac{\omega_3}{\omega_c}\right)^8 - B^2 \left(\frac{\omega_3}{\omega_c}\right)^2 - 1 = 0 \quad (5.106)$$

$$\frac{\omega_3}{\omega_s} = \sqrt{h} \frac{\omega_3}{\omega_c} \quad (5.107)$$

5.4 Graphical Tool for Enclosure Design

Small's paper used the equations for CB4 and QB3 filters to generate plots where one can find the compression ratio $\alpha = V_{as}/V_b$, box frequency $h = \omega_b/\omega_s$, speaker Q_t , and cut-off frequency ω_3/ω_s if one of those variables were known. Using the code from Appendix B, we can generate such a figure as seen in Figure 5.4. If the proper parameters are chosen, the normalized power transfer function follows Figure 5.5.

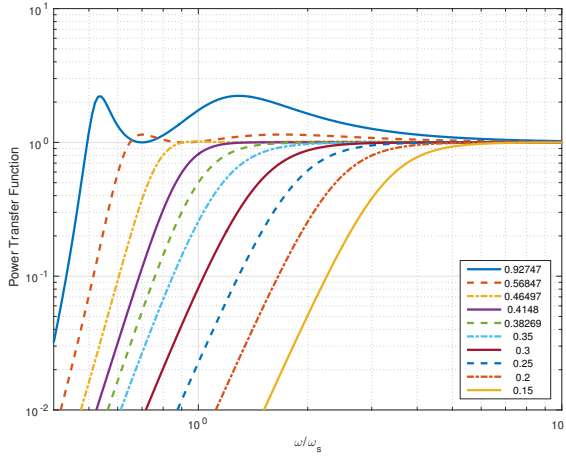


Figure 5.5: Vented box normalized power transfer function as a function of Q_{ts}

5.4.1 Closed or Vented Box?

The choice between the closed/sealed or vented/ported design is based on the available driver specifications and desired frequency response. For example, Figure 5.6 shows a comparison of performance and design values between a B2 closed box (thin lines) and a QB3-B4-C4 vented box (thick lines). Some conclusions can be drawn: (1) vented boxes always have a lower ω_3 than closed boxes for a given Q_{ts} and (2) closed boxes are smaller than vented boxes when $Q_{ts} < 0.6$.

An additional tool to aid decisions is to look at the *efficiency bandwidth product* (EBP), defined by Richard Small² as:

$$\text{EBP} = \frac{\omega_s}{2\pi Q_{es}} = \frac{f_s}{Q_{es}} \quad (5.108)$$

Prof. Small is attributed to have given the following guidelines to interpret EBP: a speaker with an $\text{EBP} > 100$ is well suited

²Commonly attributed to Small, but I have not been able to find the original citation

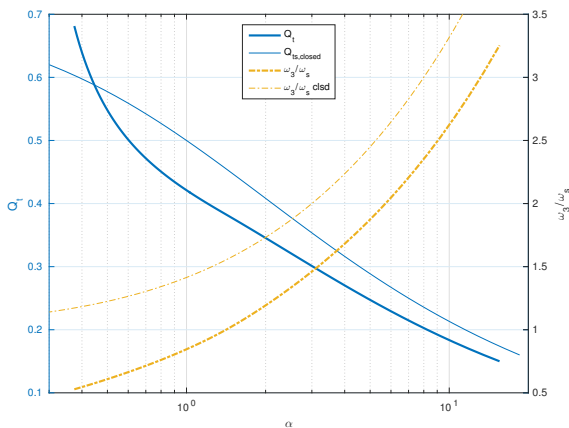


Figure 5.6: Relationship between compression ratio (α), normalized cut-off frequencies (ω_3) for a given Q_{ts} (vented box, thick lines); α , ω_3/ω_s , and Q_{ts} (closed box, thin lines)

for a ported design, $EBP < 50$ is well suited for a closed design, and $50 < EBP < 100$ could be either. This can be seen as an interpretation of Figure 5.6. If a speaker has high f_s , you want to use the ported design to get the lowest ω_c . If a speaker has a high Q_{es} and thus a high Q_{ts} , ω_c will be already be low, so using the smaller sealed box can be convenient.

5.5 Group Delay?

5.6 Excursion and Power ratings?

5.7 Efficiency

From our calculation of acoustic power Equation 5.13 with the transfer function Equation 5.18.

$$\langle P_a(\omega) \rangle = \frac{|v_o|^2 S_d^2 \rho}{4\pi c (B\ell)^2 R_e^2 C_{es}^2} \left| \hat{H}(\omega) \right|^2 \quad (5.109)$$

where $\hat{H}(\omega)$ is a function normalized to 1 when $\omega > \omega_c$. The electrical power dissipated is nearly entirely dissipated in the voice coil ($Q_{es} < Q_{ms}$), and as such the electrical power delivered is:

$$\langle P_e \rangle = \frac{|v_o|^2}{2R_e} \quad (5.110)$$

from which efficiency can be found:

$$\eta = \frac{\langle P_a \rangle}{\langle P_e \rangle} = \frac{S_d^2 \rho}{2\pi c (B\ell)^2 R_e C_{es}^2} |f(\omega)|^2 = \eta_0 |f(\omega)|^2 \quad (5.111)$$

where $f(\omega)$ is a function that becomes 1 when $\omega > \omega_c$ and η_0 is the reference efficiency:

$$\eta_0 = \frac{S_d^2 \rho}{2\pi c (B\ell)^2 R_e C_{es}^2} = \frac{\rho}{2\pi c} \frac{(B\ell)^2 S_d^2}{R_e M_{ms}^2} = \frac{4\pi f_s^3 V_{as}}{c^2 Q_{es}} \quad (5.112)$$

which is the maximum percent of electrical power available to be converted acoustic power.

5.8 Sound Power Level (SWL) and Sound Pressure Level (SPL)

Sound power level (SWL) is defined as:

$$L_W = 10 \log_{10} \left(\frac{P_a}{P_0} \right) \text{ dB} \quad (5.113)$$

where P_0 is some reference level (i.e., defines 0 dB).

Sound power is the total power output of a speaker, independent of distance from acoustic source. Another common description of speaker power is sound pressure level (SPL) $L_p = 10 \log_{10} \left(\frac{I}{I_0} \right)$, a function of the intensity of the sound wave which

is in itself a function of distance from the source. Recognizing $P_a = AI$ where A is area and I is sound intensity, sound power level can be written as:

$$L_p = 10 \log_{10} 0 \left(\frac{I}{I_0} \right) = 10 \log_{10} \left(\frac{P_a/A}{P_0/A_0} \right) \quad (5.114)$$

$$= 10 \log_{10} \left(\frac{P_a}{P_0} \right) - 10 \log_{10} \left(\frac{A}{A_0} \right) \quad (5.115)$$

$$= 10 \log_{10} \left(\frac{\eta P_e}{P_0} \right) - 10 \log_{10} \left(\frac{A}{A_0} \right) \quad (5.116)$$

$$L_p = 10 \log_{10} (\eta) + 10 \log_{10} \left(\frac{P_e}{P_0} \right) - 10 \log_{10} \left(\frac{A}{A_0} \right) \quad (5.117)$$

Reference values are chosen such that 0 dB is the smallest signal audible to a human. For this, P_0 is chosen to be the output power required to generate a pressure wave such that the amplitude of the pressure wave is 20 μ pascals when 1 m away from a reference point source when the point source radiates into a hemisphere ($A_0 = 2\pi \text{ m}^2$). The electrical power reference is chosen to be $P_e = 1 \text{ W}$, and the area of the acoustic sound is also reference to the area of a hemisphere with a radius of 1 m ($A = 2\pi \text{ m}^2$). Therefore, the SPL referenced to 1 watt electrical power dissipated and SPL measured 1 meter from the source is:

$$L_p = 10 \log_{10} (\eta) + 112.1 \text{ dB 1W 1m} \quad (5.118)$$

5.9 Including effects of loss?

5.10 Computer Design:

Given a user defined “range of interest” of frequencies (e.g., 20 Hz-20 kHz), and driver specifications, minimize RMS error of SPL given a constraint of max box size. Simultaneously optimize for two speakers (similar efficiencies).

5.10.1 Two-way Speaker Design

Optimize box for low-frequency only, but impedance match features in pass bands?

<http://www.audioholics.com/loudspeaker-design/>

cross-over 2x above fs

inductor for woofer to protect it?

efficiency Back to model - get rid of backwards waves with a big baffle, now we are delivering energy.

efficiency: simply $(v_r a d^2 / R_{rad}) / (v_{in}^2 / total R)$

The goal is to delivery energy to the acoustic transmission, can we help impedance match? elements you need for impedance match = Helmholtz resonator! get vent 180 degrees out of phase for free! Get all electrical energy on to real part (both mechanical resistance and sound). Good = more efficient, bad=what if system has bad Q? too much energy(forces) on resistors/mechanical elements? impedance mismatch with Re Le?

well designed box, minimize electronic impedance matching!

Why sealed box? impedance match mass.

efficiency is proportional to difference in voltage over res and voltage over rev (assuming vent losses are low). voltage is transferred to Q

when there is no box, $Q_b = Q_l = 0$, load is inductive and added to $M_m s$

should i make inductors all value of M?

μ for air is $1.56 \times 10^{-5} \text{m}^2/\text{s}$.

split variable definitions in to electrical mechanical acoustic Also derived variables?

EBP - compare efficiency of sealed to vented, when does one win?

references:

Website:

andyc.diy-audio-engineering.org/vented_box_2.xhtml

f3 is in small's appendices

Appendix A

random stuff

time avg power

$$\langle P_L \rangle = \lim_{T \rightarrow \infty} \int_{t=0}^{t=T} V I dt \quad (\text{A.1})$$

$$\langle P_L \rangle = \lim_{T \rightarrow \infty} \int_{t=0}^{t=T} \Re\{\hat{v}_L e^{i\omega t}\} \Re\left\{\frac{\hat{v}_L}{\hat{Z}_L} e^{i\omega t}\right\} dt \quad (\text{A.2})$$

$$\langle P_L \rangle = \int_{t=0}^{t=\frac{2\pi}{\omega}} |\hat{v}_L| \cos(\omega t + \phi_v) \left(\frac{|\hat{v}_L|}{|\hat{Z}_L|} \cos(\omega t + \phi_v - \phi_{\hat{Z}_L}) \right) dt \quad (\text{A.3})$$

$$\langle P_L \rangle = \frac{|\hat{v}_L|^2}{2 |\hat{Z}_L|} \cos \phi_{\hat{Z}_L} = |\hat{v}_0|^2 \frac{|\hat{Z}_L|}{2 |R_g + \hat{Z}_L|^2} \cos \phi_{\hat{Z}_L} \quad (\text{A.4})$$

where $\hat{Z}_L = |\hat{Z}_L| e^{i\phi_{\hat{Z}_L}}$.

A.1 excursion? Max power?

Appendix B

QB3, C4 Alignment Code